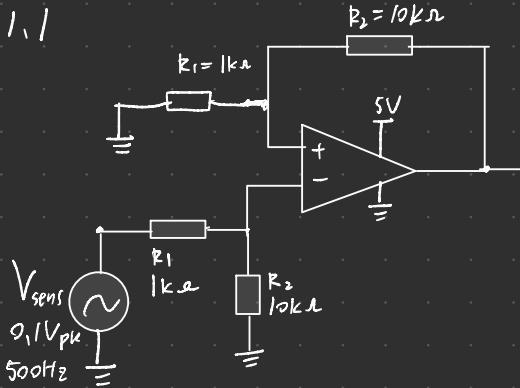


Q 1.1



$$V^- = V^+ = V_{\text{sens}} \times \frac{R_2}{R_2 + R_1}$$

$$\frac{V_{\text{out}} - V^+}{R_2} = \frac{V^+ - 0}{R_1}$$


$$V_{\text{out}} = \frac{R_2}{R_1} V^+ + V^+$$

$$V_{\text{out}} = V_{\text{sens}} \frac{R_2}{R_2 + R_1} \left(\frac{R_1}{R_2} + 1 \right)$$


$$V_{\text{out}} = 10 V_{\text{sens}}$$

$$A_v = \frac{V_{\text{out}}}{V_{\text{sens}}} = 10$$

Theoretical

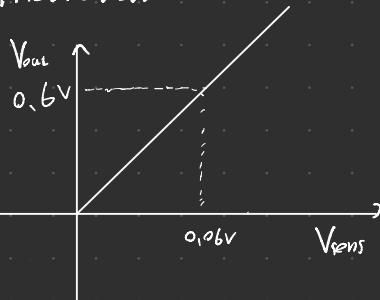

Simulated

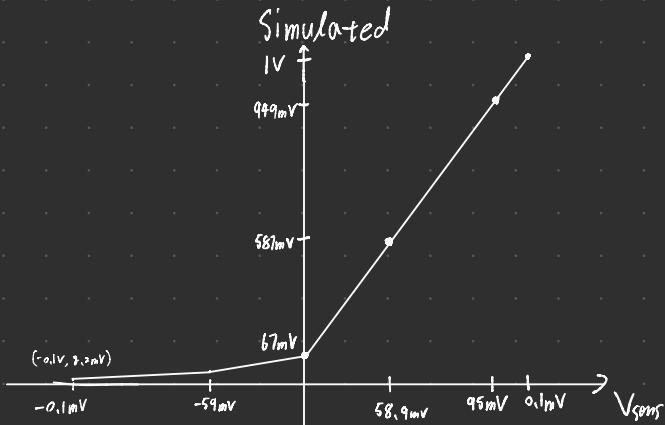


Q1.3


In the OpAmp_LM324 data sheet page 7/22.

Symbol	Parameter	Min.	Typ.	Max.	Unit
V _{OH}	High level output voltage, V _{CC} = 30 V, R _L = 2 kΩ	26	27		
	T _{amb} = 25 °C				
	T _{min} ≤ T _{amb} ≤ T _{max}	26			
	High level output voltage, V _{CC} = 30 V, R _L = 10 kΩ	27	28		V
	T _{amb} = 25 °C				
V _{OL}	T _{min} ≤ T _{amb} ≤ T _{max}	27			
	High level output voltage, V _{CC} = 5 V, R _L = 2 kΩ	3.5			
I _{OL}	T _{amb} = 25 °C				
	T _{min} ≤ T _{amb} ≤ T _{max}	3			

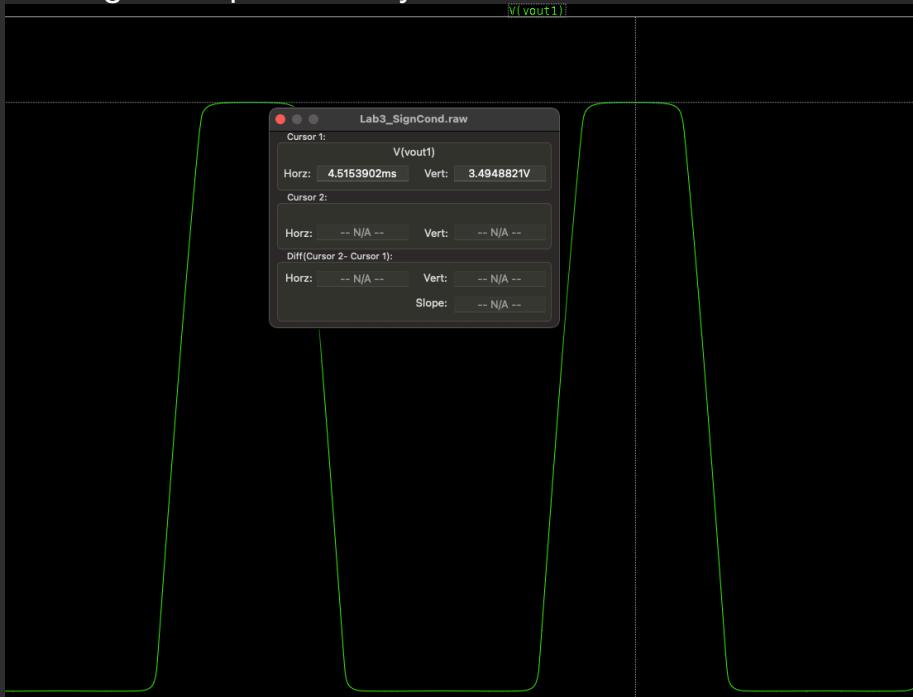I changed the Vsens form 0.1 to 0.5 at LTspice and measure it's output voltage. The peak is very close to 3.5V.



Q 1,5

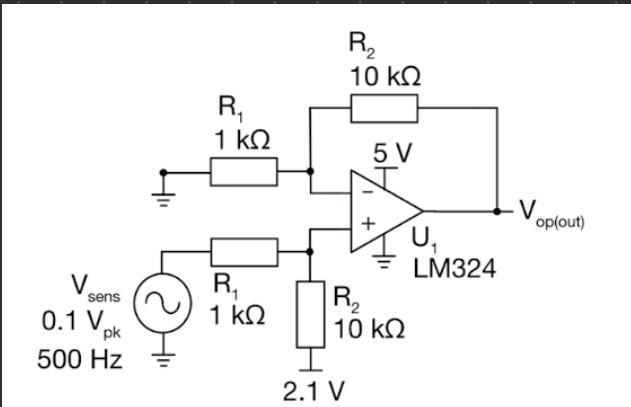

$$\frac{V_{\text{sens}} - V^+}{R_1} = \frac{V^+ - 2.1}{R_2}$$


$$\frac{V_{\text{sens}}}{R_1} - \frac{V^+}{R_1} = \frac{V^+}{R_2} - \frac{2.1}{R_2}$$

$$V^+ \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{\text{sens}}}{R_1} + \frac{2.1}{R_2}$$

$$V^+ = \frac{10}{11} \left(V_{\text{sens}} + \frac{2.1}{10} \right)$$

$$\frac{V_{\text{out}} - V^-}{10} = \frac{V^-}{1} \quad V^+ = V^-$$
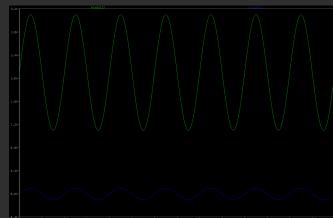
$$V_{\text{out}} = 10V^- + V^- = 11V^- = 10V_{\text{sens}} + 2.1$$




Q2.1

Calculated in Lab 1:

$$R_s = 0.5 \quad , \quad I_{L(\text{rms})\text{max}} = 595.238 \text{ mA}$$

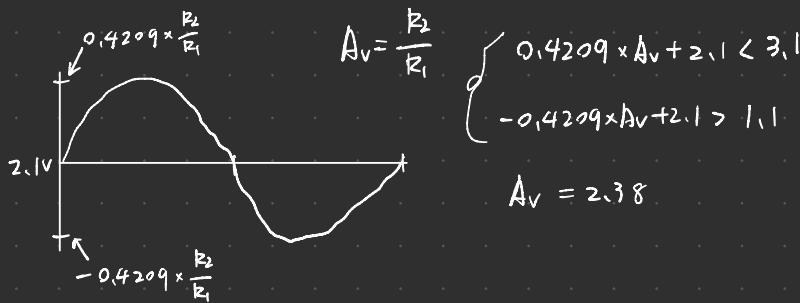Based on Ohm's law: $V_{is(pk)\text{max}} = 595.238 \times 10^{-3} \times 0.5 \times \sqrt{2} = 0.4209 \text{ V}$




I selected $R_1 = 10 \text{ k}\Omega$ and $R_2 = 22 \text{ k}\Omega$, it results Av in 2.2.

Checking the AC voltage range:

$$0.4209 \times 2.2 + 2.1 = 3.025 < 3.1 \quad (\text{passed})$$
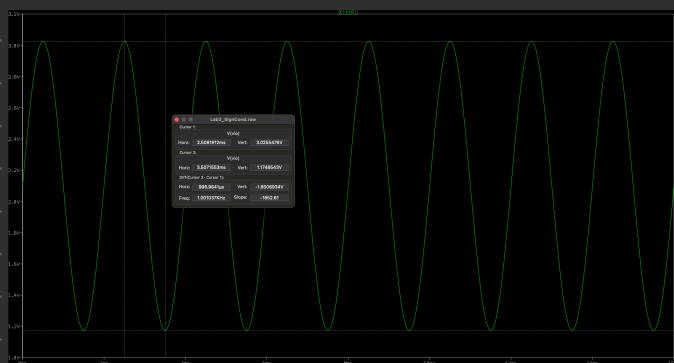
$$-0.4209 \times 2.2 + 2.1 = 1.174 > 1.1 \quad (\text{passed})$$



Q 2.2

(7.5VA at 12.6V)

$$I_L(\text{rms}) = 595.238 \text{ mA}$$

$$V_{is(pk)} = 595.238 \times 10^{-3} \times 0.5 \times \sqrt{2} = 0.4209 \text{ V}$$

$$V_{io(pk)} = 0.4209 \times 2.2 + 2.1 = 3.9260 \text{ V}$$

(7.5VA at 15.4V)

$$I_L(\text{rms}) = 484.013 \text{ mA}$$

$$V_{is(pk)} = 484.013 \times \sqrt{2} \times 10^{-3} \times 0.5 = 0.3422 \text{ V}$$

$$V_{io(pk)} = 0.3422 \times 2.2 + 2.1 = 2.8529 \text{ V}$$

(2.5VA at 15.4V)

$$I_L(\text{rms}) = 162.3377 \text{ mA}$$

$$V_{is(pk)} = 162.3377 \times 10^{-3} \times \sqrt{2} \times 0.5 = 0.1148 \text{ V}$$

$$V_{io(pk)} = 0.1148 \times 2.2 + 2.1 = 2.3525 \text{ V}$$

Q 2.3

$$V_{out} = \frac{R_2}{R_1} (V^+ - V^-) \quad V^+ = V^- = V_{cm} \left(\frac{\frac{R_4}{R_3}}{R_3 + R_4} \right)$$

$$\frac{V_{cm} - V^-}{R_1} = \frac{V^- - V_{out}}{R_3} \Rightarrow V_{out} = V^- \left(\frac{R_1 + R_3}{R_1} \right) - V_{cm} \left(\frac{R_3}{R_1} \right)$$

$$V_{out} = V_{cm} \left(\frac{\frac{R_4}{R_3 + R_4}}{\frac{R_2 + R_4}{R_1}} \right) \left(\frac{\frac{R_1 + R_3}{R_1}}{\frac{R_3}{R_1}} \right) - V_{cm} \left(\frac{\frac{R_3}{R_1}}{\frac{R_3}{R_1}} \right)$$

$$A_{cm} = \left(\frac{\frac{R_4}{R_3 + R_4}}{\frac{R_2 + R_4}{R_1}} \right) \left(\frac{\frac{R_1 + R_3}{R_1}}{\frac{R_3}{R_1}} \right) - \left(\frac{R_3}{R_1} \right) \quad \text{and if } \frac{R_3}{R_1} = \frac{R_4}{R_2}, A_{cm} \text{ will be zero.}$$


Q3.1 $R_a = 1 \text{ k}\Omega$ and $R_b = 20 \text{ k}\Omega$ and $V_{vs(\text{lab})} = 1.0371 \text{ V}$ from Lab 1

V_o supposed to be $1 \text{ V}_{(\text{PUI})}$

$V_v = \frac{1 \text{ V}}{1.0371 \text{ V}} = 0.9642$ which is very close to 1,

so I picked $R_{1a} = 10 \text{ k}\Omega$, $R_{1b} = 10 \text{ k}\Omega$, and $R_2 = 10 \text{ k}\Omega$

Q3.2

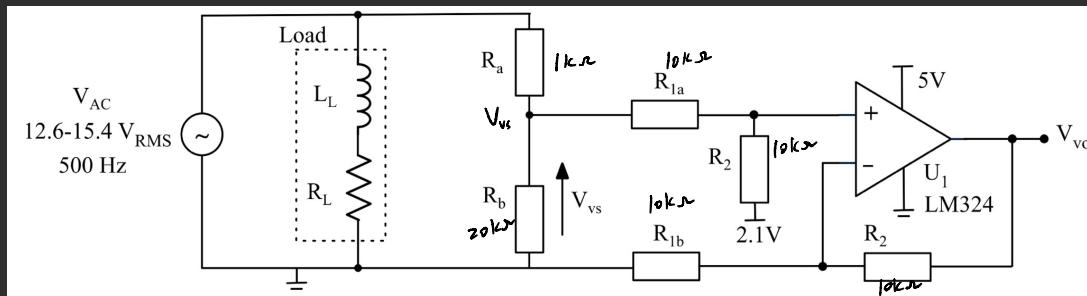

$$V_{vo} = V_{vs} + 2.1$$

(7.5VA at 12.6v)

$$V_{vs} = 0.8485 \text{ V} \quad A_V = 1$$

$$V_{vo} = 0.8485 \times 1 + 2.1 = 2.9484 \text{ V}$$

(7.5VA at 15.4)

$$V_{vs} = 1.0371 \text{ V} \quad A_V = 1$$

$$V_{vo} = 1.0371 + 2.1 = 3.1371 \text{ V}$$

(2.5VAC at 15.4V)

$$V_{vs} = 1.0371 \text{ V} \quad V_{vo} = 1.0371 + 2.1 = 3.1371 \text{ V}$$

Q 4.1


$$\frac{V_{\text{filter}}}{V_{\text{opamp}}} = \frac{Z_c}{R_f + Z_c} = \frac{\frac{1}{j\omega C}}{R_f + \frac{1}{j\omega C}} = \frac{1}{j\omega C} \times \frac{j\omega C}{1 + j\omega C R_f} = \frac{1}{1 + j\omega C R_f}$$

$$f_b = 10 \text{ kHz} = \frac{1}{2\pi R_f C_f}$$

$$\text{I picked } R_f = 1 \text{ k}\Omega \longrightarrow C_f = \frac{1}{10 \times 10^3 \times 2\pi \times 10^3} = 15.91 \text{ nF}$$

This is a sweet spot, which avoiding noise and ADC issue. Also, the op-amp isn't overloaded.

Q4.2

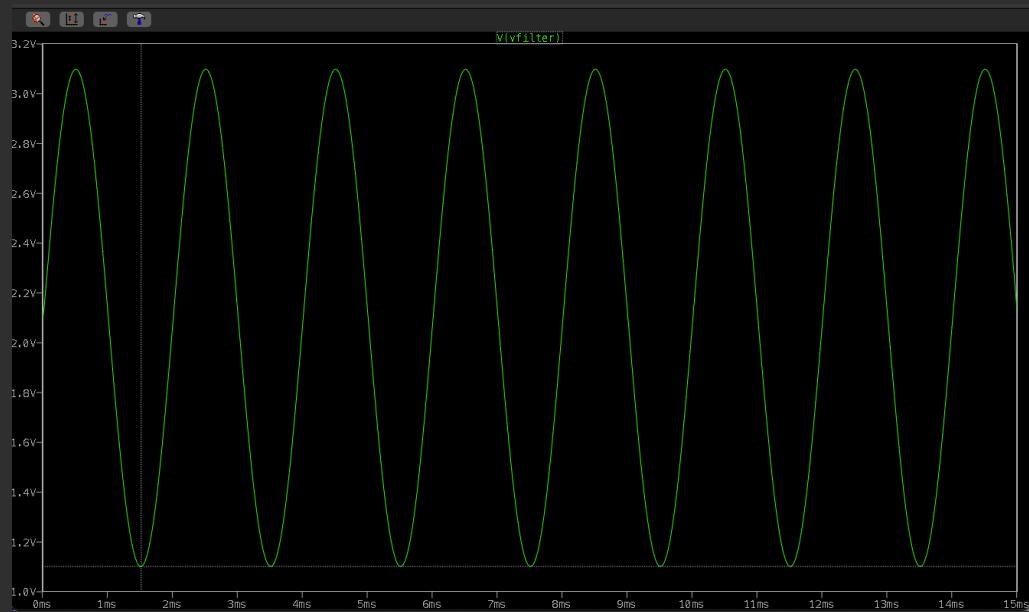

Q 4.3

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \sqrt{1 + (\omega RC)^2} \quad \angle H(j\omega) = -\tan^{-1}(\omega RC)$$





At f_b , Gain = -3 dB and Phase = -45° $f_b = \frac{1}{2\pi RC} = 10610.23954 \text{ Hz}$

f	$H(j\omega)$	$\angle H(j\omega)$
100 Hz	-0.00038 dB	0.5399°
1k Hz	-0.038 dB	5.3841°
10k Hz	-2.76 dB	43.3040°
100 kHz	-19.53 dB	83.9434°
1MHz	-39.48 dB	89.3921°

$$\text{Gain (dB)} = 20 \log \left(\frac{1}{\sqrt{1 + \left(\frac{f}{f_b} \right)^2}} \right)$$

$$\phi = -\tan^{-1} \left(\frac{f}{f_b} \right)$$

Q4.4

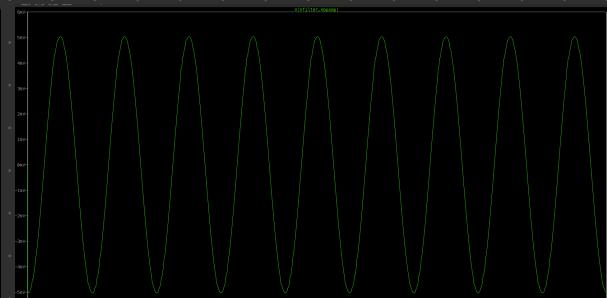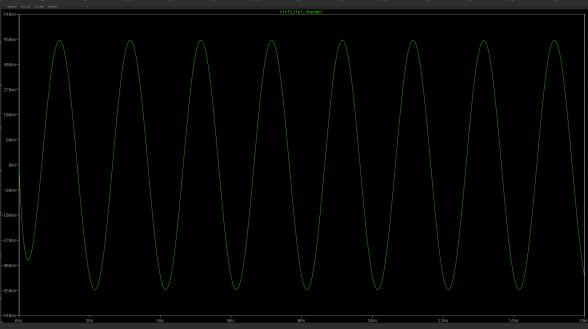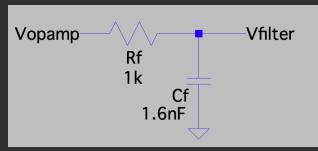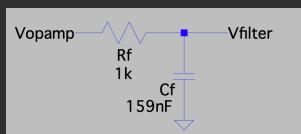


Q5.1




$$\Delta V_{in} = \frac{I_{reg} \cdot \Delta t}{C_s} = \frac{0.05 \times 0.002}{47 \times 10^{-6}} = 2.1276 \text{ V}$$

Q5.3


Part 5

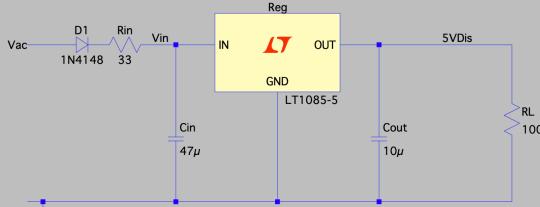

Part 5

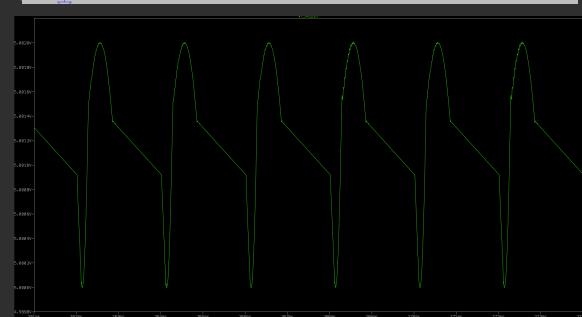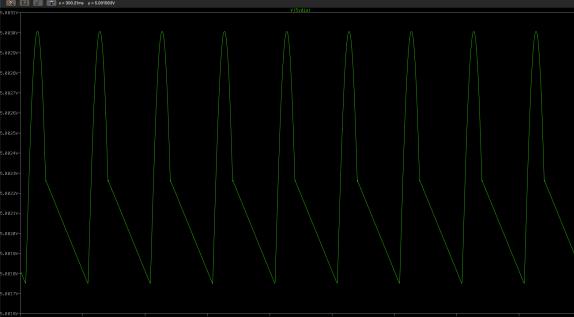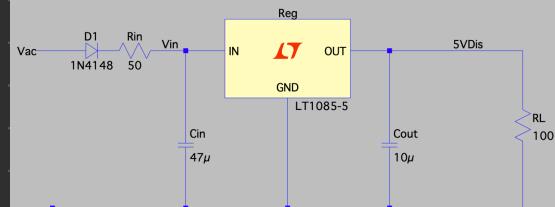

Q5.5

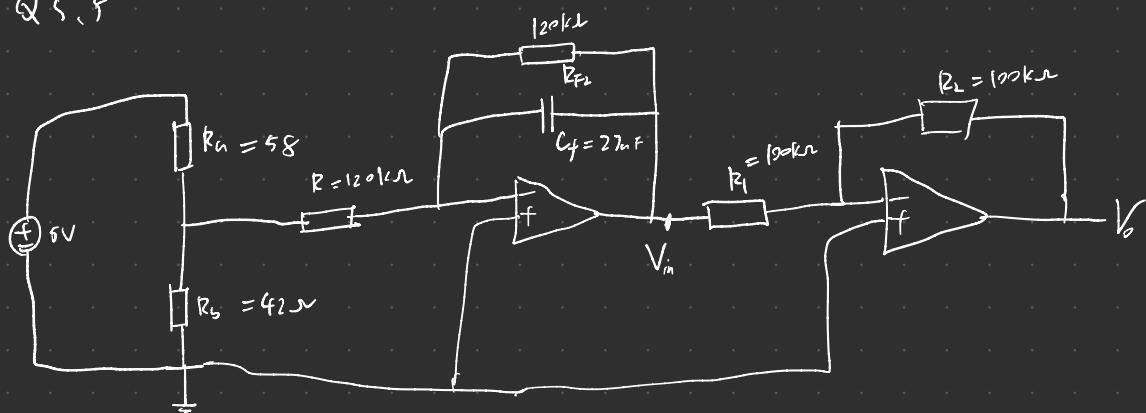

$$2.1 = 5 \times \left(\frac{R_1}{R_a + R_b} \right) \quad \frac{2.1}{5} = \frac{\dot{B}_b}{R_a + R_b} \quad \frac{5}{2.1} = \frac{R_o}{R_a} + 1$$

$$\frac{\dot{B}_b}{R_a} = \frac{29}{21} \quad \dot{B}_b = 42 \text{ V} = 39 + 1.5 + 1.5$$

$$R_a = 58 \text{ ohm} = 56 + 1 + 1$$

$$\text{For DC, } -1 = -\frac{R_{F1}}{R_{T2}} \rightarrow F_{F1} = F_2$$

$$f = 50 \text{ Hz} \Rightarrow \omega_b = 2\pi \cdot 50 \text{ rad/s}$$

$$C = \frac{1}{2\pi \cdot 50 \times R_{F2}}$$

$$I \text{ picked } R_{F2} = 120\text{k}\Omega \text{ so } C = 26.52\text{nF} \approx 27\text{nF}$$

$R_1 = R_2 = 100\text{k}\Omega$ for inverting -2.1V to positive