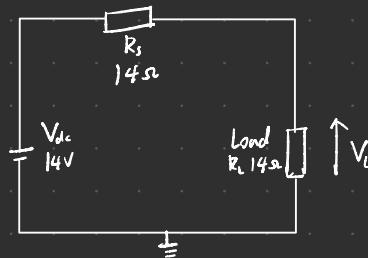


Q 1.1



$$I_L = \frac{14}{14+14} = 0.5 \text{ A}$$

$$V_L = 14 \times \frac{14}{14+14} = 7 \text{ V}$$

$$P_L = I_L^2 \times R_L = 0.5^2 \times 14 = 3.5 \text{ W}$$

Q 1.2

Theoretical	Simulated
I_L	0.5 A
V_L	7 V
P_L	3.5 W


The theoretical and simulated results are matched.

Q 1.3


$$\text{Stop Time: } 200 \times 2 \text{ ms} = 0.4 \text{ s}$$

$$\text{Max timestamp: } \frac{1}{20} \times \frac{1}{500} = 0.1 \text{ ms}$$

Q 1.4

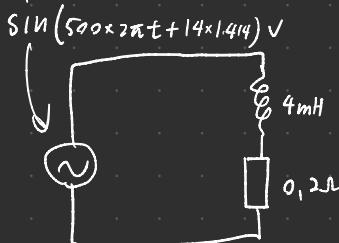

$$\tau = \frac{L}{R} = 0.02 \text{ s}$$

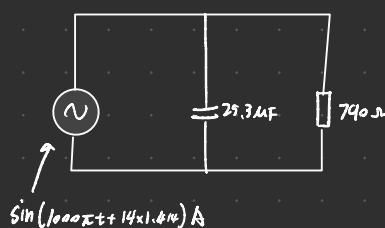


$$\tau = RC = 0.019987 \text{ s}$$

Both will reach steady-state before defined stop time, 0.4s

Q1.5

ignoring the added resistances.

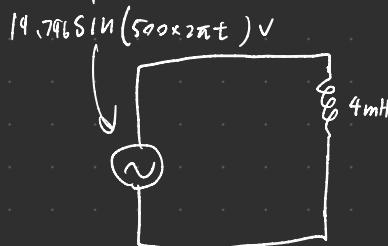


$$X_L = 2\pi \times 500 \times 0.004 = 12.57 \Omega$$

$$I_{RMS} = \frac{14}{12.57} = 1.11 A$$

V_{RMS} is given $V_{RMS} = 14 V$

$$P_{L(t)} = \frac{14.796 \times 1.11}{2} = 15.609 W$$

$P_{avg} = 0$ Cuz of its ideal inductor.

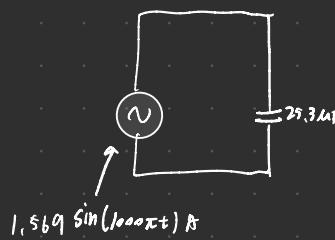

$$1.569 \sin(1000\pi t) V$$

$$I_{RMS} = 1.11 A$$


$$X_C = \frac{1}{\omega C} = \frac{1}{3141.6 \times 25.3 \times 10^{-6}} = 12.5814 \Omega$$

$$I_{L RMS} = 1.11 A$$

$$V_{L(RMS)} = I_{L(RMS)} \times X_L = 13.9654 V$$

$$P_{L(t)} = I_{RMS} \times V_{RMS} \times \cos(90^\circ) = 15.502 W$$

$$P_{avg} = 0 \text{ (ideal inductor)}$$

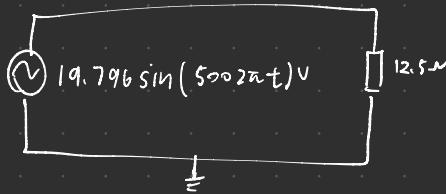



$$I_{RMS} = \frac{V_{RMS}}{R} = \frac{14}{12.5} = 1.12 A$$

V_{RMS} is give, $V_{RMS} = 14 V$


$$P_{in} = V_{RMS} \times I_{RMS} = 14 \times 1.12 = 15.68 W$$

$$P_{L(t)} = 14 \times 12 \times 1.12 \times 12 = 31.36 W$$

Q 1.6

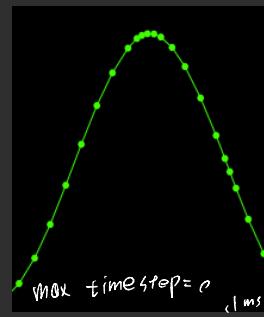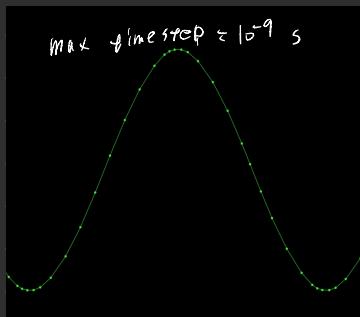


Q 1.7

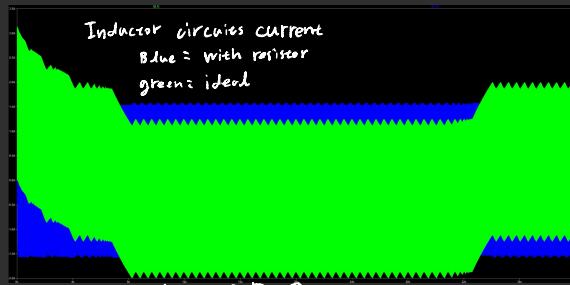

$$\text{For ideal: } \tau = R = 0$$
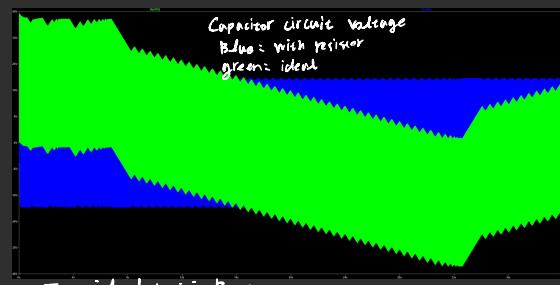
$$\therefore \tau = \frac{L}{R} = \frac{L}{0} = \infty$$



$$\text{For ideal: } \tau = C = 0$$


$$\therefore \tau = C \times 0 = 0$$

Q 2.1

$$I_{\max} = \frac{7.5 \text{ VA}}{12.6 \text{ V}} = 595.2381 \text{ mA}$$

$$I_{\min} = \frac{2.5 \text{ VA}}{15.4 \text{ V}} = 162.3377 \text{ mA}$$

Q 2.2

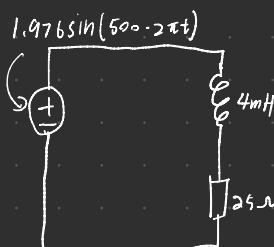

$$X_L = 2\pi \times 500 \times 4 \times 10^{-3} = 12.5664 \Omega$$

$$Z_L = \sqrt{25^2 + 12.5664^2} = 27.9806 \Omega$$

$$I_{L(\text{RMS})} = \frac{V_{\text{ac(RMS)}}}{Z_L} = \frac{14}{27.9806} = 500.3465 \text{ mA}$$

$$|S| = 14 \times 500.3465 \times 10^{-3} = 7.0049 \text{ VA}$$

$$P = 25 \times (500.3465 \times 10^{-3})^2 = 6.2587 \text{ W}$$

$$Q = 12.5664 \times (500.3465 \times 10^{-3})^2 = 3.1459 \text{ VAR}$$

Simulated RMS voltage: 13,877 V

Simulated RMS current: 494,24 mA

$$|S_{\text{simulated}}| = 13,877 \times 494,24 \times 10^{-3} = 6,8586 \text{ VA}$$

$$Q_{\text{simulated}} = \sqrt{S_{\text{simulated}}^2 - P_{\text{simulated}}^2} = \sqrt{6,8586^2 - 61174^2} = 3,1013 \text{ VAR}$$

Q2.3

$$X_L = 12,5664 \Omega \quad Z_L = \sqrt{12,5664^2 + 75^2} = 76,0455 \Omega$$

$$I_L(\text{RMS}) = \frac{14}{76,0455} = 184,1 \text{ mA}$$

$$|S| = 14 \times 184,1 \times 10^{-3} = 2,5774 \text{ VA}$$

$$P = (184,1 \times 10^{-3}) \times 75 = 2,542 \text{ W}$$

$$Q = (184,1 \times 10^{-3})^2 \times 12,5664 = 0,4259 \text{ VAR}$$

$$I_{L(\text{RMS}) \text{ simulated}} = 182,35 \text{ mA} \quad V_{L(\text{RMS}) \text{ simulated}} = 13,875 \text{ V}$$

$$P_{\text{simulated}} = 2,4948 \text{ W} \quad |S_{\text{simulated}}| = 13,875 \times 182,35 \times 10^{-3} = 2,5301 \text{ VA}$$

$$Q_{\text{simulated}} = \sqrt{2,5301^2 - 2,4948^2} = 0,4212 \text{ VAR}$$

Q 3.1

Identifying the constraint:

$$I_{\max} = 595,2381 \text{ mA} \quad \text{and} \quad P_{\max} = 0,2 \text{ W}$$

Calculate $P_{S(\max)}$:

$$R_{S(\max)} = \frac{P_{\max}}{I^2} = \frac{0,2}{(595,2381 \times 10^{-3})^2} = 0,5645 \Omega$$

Q 3.2

(Scenario 1: 7.5 VA at 12.6 V)

$$I_{L(RMS)} = \frac{7.5 \text{ VA}}{12.6 \text{ V}} = 595,2381 \text{ mA}, \quad X_L = 2\pi \times 500 \times 0,004 = 12,5664 \Omega$$

$$\text{Total impedance required: } |Z_{\text{total}}| = \frac{12.6 \text{ V}}{595,2381 \times 10^{-3}} = 21,168 \Omega$$

$$|Z_{\text{total}}|^2 = R_L^2 + X_L^2$$

$$R_L = \sqrt{|Z_{\text{total}}|^2 - X_L^2} = \sqrt{21,168^2 - 12,5664^2} = 17,0344 \Omega$$

$$V_{pk(\text{Theo})} = I_{L(RMS)} \times R_S \times \sqrt{2} = 595,2381 \times 0,5645 \times 10^{-3} \times \sqrt{2} = 0,4752 \text{ V}$$

$$P_{is} = P_{\max} = (595,2381 \times 10^{-3})^2 \times 0,5645 = 0,2 \text{ W}$$

(Scenario 2: 7.5 VA at 15.4 V)

$$I_{L(RMS)} = \frac{7.5 \text{ VA}}{15.4 \text{ V}} = 484,013 \text{ mA}$$

$$R_L = \sqrt{31,6213^2 - 12,5664^2} = 29,2306 \Omega$$

$$|Z_{\text{total}}| = \frac{15.4 \text{ V}}{484,013 \times 10^{-3}} = 31,8173 \Omega$$

$$V_{is(\text{Theo})} = 484,913 \times 10^{-3} \times 0,5645 \times \sqrt{2} = \underline{\underline{2,3864 \text{ V}}}$$

$$P_{is(\text{Theo})} = (484,913 \times 10^{-3})^2 \times 0,5645 = \underline{\underline{0,1322 \text{ W}}}$$

(Scenario 3: 2.5 VA at 15.4 V)

$$I_L(z_{rms}) = \frac{2.5 \text{ VA}}{15.4 \text{ V}} = \underline{\underline{162,3377 \text{ mA}}} \quad |Z_{\text{total}}| = \frac{15.4}{162,3377 \times 10^{-3}} = 94,864 \Omega$$



$$R_L = \sqrt{94,864^2 - 12,5664^2} = 94,028 \Omega$$

$$V_{is(\text{Theo})} = 162,3377 \times 10^{-3} \times 0,5645 \times \sqrt{2} = 0,1296 \text{ V}$$

$$P_{is(\text{Theo})} = (162,3377 \times 10^{-3})^2 \times 0,5645 = 0,01488 \text{ W}$$

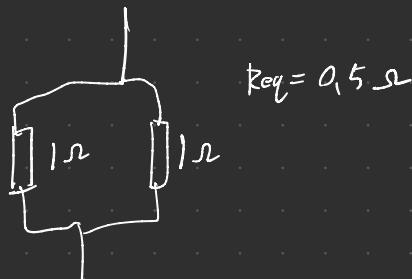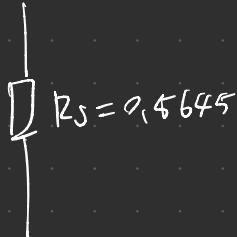Q 3.3

Because the minimum resistor we can find in the lab is 1 ohm, so we need to use two resistors in parallel to approach to 0.5685



Q 4.1

In Q2.1, I have calculated that max input voltage is $15.4 \text{ V}_{\text{rms}}$.

Target output voltage should be 2V (peak-to-peak), ie means

$V_{\text{out(pk)}}$ should be 1V.

$$V_{\text{in(pk)}} = 15.4 \times \sqrt{2} = 21.7789 \text{ V}$$

$$V_{\text{out}} = V_{\text{in}} \times \frac{R_b}{R_a + R_b} \quad \text{and} \quad \text{Ratio} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{r}{21.7789} = 0.04592 = \frac{R_b}{R_a + R_b}$$

$$0.04592 R_a + 0.04592 R_b = R_b \Rightarrow 0.04592 R_a = 0.9541 R_b$$

$$\frac{R_a}{R_b} = \frac{0.9541}{0.04592} = \underline{\underline{20.7771}}$$

I pick $R_b = \underline{\underline{4.7k\Omega}}$ because it's large enough to limit power dissipation.

$$\text{Given that } \frac{R_a}{R_b} = 20.7771, \quad R_a \approx 97.65237 \text{ k}\Omega$$

So I choose an E2 resistor close to $97.65237 \text{ k}\Omega \Rightarrow R_a = 100 \text{ k}\Omega$

$$\text{Check: } V_{\text{out(pk)}} = 21.7789 \times \frac{4.7k}{104.7k} = 0.977$$

However, my teammate proposed a better resistor combination, which is $R_a = 20 \text{ k}\Omega$ and $R_b = 1 \text{ k}\Omega$.

It turned out the $\frac{R_a}{R_b}$ to be ≈ 20

$$\text{And the output voltage will be: } V_{\text{out(pk)}} = 21.7789 \times \frac{1}{21} = 1.0371$$

It slightly more deviate from 1V than 0.977 but it will be easier for calculation in the following design.

Q4.2 I've picked that $R_a = 100k\Omega$ and $R_b = 4.7k\Omega$

(Scenario 1: 7.5VA at 12.6V)

$$V_{ac(rms)} = 12.6 \times \sqrt{2} = 17.8191V$$

R_L is calculated, $R_L = 16.4699\Omega$

$$\text{Peak Voltage, } V_{vs(\text{pk, theo})} = 17.8191 \times \frac{1}{21} = \underline{\underline{0.8485V}}$$

$$\text{Power Dissipation, } P_{vs} = \frac{V^2}{R_a + R_b} = \frac{12.6^2}{21k} = \underline{\underline{7.56mW}}$$

$$P_{b(sim)} = 6.6955mW \quad P_{vs(sim)} = P_{b(sim)} + P_{a(sim)} = \underline{\underline{7.0090mW}}$$

$$P_{a(sim)} = 313.48 \times 10^{-3} mW$$

(Scenario 2: 7.5VA at 15.4V)

$$V_{ac(rms)} = 15.4 \times \sqrt{2} = 21.7789V \quad V_{vs(\text{pk})} = 21.7789 \times \frac{1}{21} = \underline{\underline{1.0371V}}$$

$$P_{vs(\text{theo})} = \frac{15.4^2}{21k} = \underline{\underline{11.2933mW}}$$

$$P_{a(sim)} = 9.9925mW \quad P_{vs(sim)} = P_{a(sim)} + P_{b(sim)} = \underline{\underline{10.4602mW}}$$

$$P_{b(sim)} = 467.66 \times 10^{-3} mW$$

(Scenario 3: 2.5VA 15.4V)

$$V_{ac(rms)} = 15.4 \times \sqrt{2} = 21.7781V \quad V_{vs(\text{pk})} = 21.7781 \times \frac{1}{21} = \underline{\underline{1.0371}}$$

$$P_{vs(\text{theo})} = \frac{15.4^2}{21k} = \underline{\underline{11.2933mW}}$$

$$P_{a(sim)} = 10.012mW \quad P_{vs(sim)} = P_{a(sim)} + P_{b(sim)} = \underline{\underline{10.4780}}$$

$$P_{b(sim)} = 468.99 \times 10^{-3} mW$$

